

CSE 4207 CT 4 Assignment
Roll No: 1903113

Assignment Problem:

Category: C

Word Size = 6

ALU Operations = ADD, OR_XOR_AND

Solution:

Video:

Have you uploaded the video?	YES
Check List 1: Have you explained the design using testbenches to prove that your circuit is working correctly and giving correct results?	YES
Check List 2: Have you shown full synthesis results showing all the required info including RTL Synthesis, RTL Floorplan, RTL Power Analysis, GDS and Heatmap (for details, see assignment template doc)?	YES
NB: Failing to upload video will cause heavy point penalty (5-6 Marks)	
NB: Failing to add any required info will cause point penalty (1-2 Marks)	

HDL Code:

Check List: Have you added all the modules written in verilog including ALU, ALU_OP1, ALU_OP2, CONTROLLER, TOP, TOP_TESTBENCH, ALU_TESTBENCH, CONTROLLER_TESTBENCH?	YES
NB: Failing to add any required info will cause point penalty (1-2 Marks)	

[Google Drive link for the files:](#)

📁 19CT4Assignment_codes_1903113

alu.v

```
module ALU
(
    input wire [5:0] A, B,
    input wire [1:0] OP,
    output wire [5:0] R,
    output wire alu_flag
);

    reg [5:0] result;
    wire [5:0] R_ADD, XOR;
```

```

wire CF_ADD;

// Instantiate modules
ALU_ADD_SUB_Nbit  ADD_SUB1(A,B,R_ADD,CF_ADD);

OR_XOR_AND_Nbit OR_XOR_AND1 (A,B,XOR);

always @(*)
begin
    case (OP)
        2'b00: // Addition
            begin
                result = R_ADD;
            end
        2'b01: // OR_XOR_AND
            begin
                result = XOR;
            end
        default:
            begin
                result = 6'b000000;
            end
    endcase
end
assign R = result;
assign alu_flag = (result > 6'b0);
endmodule

```

alu_op1.v

```

module OR_XOR_AND_Nbit
(
    input wire [5:0] A,B,
    output wire [5:0] R
);

    assign R = ((A|B)^(A&B));

endmodule

```

alu_op2.v

```

module ALU_ADD_SUB_Nbit
(
    input wire [5:0] A,B,
    output wire [5:0] R,
    output wire CF

```

```
);

    assign {CF, R} = A + B;

endmodule
```

controller.v

```
module controller
(
    input wire clk, reset, start,
    input wire [5:0] a, b,
    input wire [1:0] op,

    input wire [5:0] alu_out,
    input wire alu_flag,
    output wire [5:0] alu_in1, alu_in2,
    output wire [1:0] alu_op,

    output reg [5:0] result,
    output reg flag
);

reg [2:0] pstate, nstate;

parameter [2:0] START = 3'b000,
                ONE = 3'b001,
                TWO = 3'b010,
                THREE = 3'b011,
                FINISH = 3'b100;

//Memory
always @(posedge clk, posedge reset)
begin : PSR
    if (reset)
        begin
            pstate <= START;
        end
    else
        begin
            pstate <= nstate;
        end
end

//Next State Logic
always @(*)
```

```

begin: NSOL
    // Monitor output
    if(pstate == START)
        $monitor("pstate = START -> clk = %b, reset = %b,
start = %b, a = %d, b = %d, op = %b, result = %d, flag =
%b\n*****\n", clk, reset,
start, a, b, op, result, flag);
    else if(pstate == ONE)
        $monitor("pstate = ONE -> clk = %b, reset = %b, start
= %b, a = %d, b = %d, op = %b, result = %d, flag =
%b\n*****\n", clk, reset,
start, a, b, op, result, flag);
    else if(pstate == TWO)
        $monitor("pstate = TWO -> clk = %b, reset = %b, start
= %b, a = %d, b = %d, op = %b, result = %d, flag =
%b\n*****\n", clk, reset,
start, a, b, op, result, flag);
    else if(pstate == THREE)
        $monitor("pstate = THREE -> clk = %b, reset = %b,
start = %b, a = %d, b = %d, op = %b, result = %d, flag =
%b\n*****\n", clk, reset,
start, a, b, op, result, flag);
    else if(pstate == FINISH)
        $monitor("pstate = FINISH -> clk = %b, reset = %b,
start = %b, a = %d, b = %d, op = %b, result = %d, flag =
%b\n*****\n", clk, reset,
start, a, b, op, result, flag);

    nstate = pstate;

    // Next State Logic and Output Logic
begin: NSL
    case (pstate)
        START:
            begin
                if (start)
                    nstate = ONE;
            end

        ONE:
            begin
                nstate = TWO;
            end

        TWO:
            begin
                nstate = THREE;
            end
    endcase
end

```

```

        end

        THREE:
        begin
            nstate = FINISH;
        end

        FINISH:
        begin
            nstate = FINISH;
        end

        default:
            nstate = START;
    endcase
end
    result = 6'b000000;
    flag = 1'b0;
begin: OL
    case (pstate)
        START:
        begin
            result = 6'b0;
            flag = 0;
        end

        ONE:
        begin
            result = alu_out;
            flag = alu_flag;
        end

        TWO:
        begin
            result = alu_out;
            flag = alu_flag;
        end

        THREE:
        begin
            result = alu_out;
            flag = alu_flag;
        end

        FINISH:
        begin
            result = alu_out;

```

```

        flag = alu_flag;
    end
    default:
        nstate = START;
    endcase
end
end

assign alu_in1 = a;
assign alu_in2 = b;
assign alu_op = op;

endmodule

```

top.v

```

module top
(
    input wire clk, reset, start,
    input wire [5:0] a, b,
    input wire [1:0] op,
    output wire [5:0] result,
    output wire flag
);

wire [5:0] alu_in1, alu_in2;
wire [1:0] alu_op;
wire [5:0] alu_out;
wire alu_flag;

controller controller1
(
    .clk(clk),
    .reset(reset),
    .start(start),
    .a(a),
    .b(b),
    .op(op),
    .alu_in1(alu_in1),
    .alu_in2(alu_in2),
    .alu_op(alu_op),
    .alu_out(alu_out),
    .alu_flag(alu_flag),
    .result(result),
    .flag(flag)
);

```

```

ALU datapath1
(
    .A(alu_in1),
    .B(alu_in2),
    .OP(alu_op),
    .R(alu_out),
    .alu_flag(alu_flag)
);

endmodule

```

top_testbench.v

```

`timescale 1ns/1ns

module top_tb;

reg clk, reset, start;
reg [5:0] a, b;
reg [1:0] op;
wire [5:0] result;
wire flag;

top top1
(
    .clk(clk),
    .reset(reset),
    .start(start),
    .a(a),
    .b(b),
    .op(op),
    .result(result),
    .flag(flag)
);

initial begin
    clk = 0;
    forever #5 clk = ~clk; // Toggle clk every 5 time units
end

initial begin
    $dumpfile("top_test.vcd");
    $dumpvars(0, top_tb);

    clk <= 0;
    reset <= 0;

```

```

    start <= 0;
    a <= 0;
    b <= 0;
    op <= 0;

    @(negedge clk);
    reset <= 1;

    @(negedge clk);
    reset <= 0;
    start <= 1;
    a <= 5;
    b <= 3;
    op <= 2'b00; // Addition: 5 + 3 = 8 (flag = 1)
    #15;

    a <= 0;
    b <= 0;
    op <= 2'b00; // Addition: 0 + 0 = 0 (flag = 0)
    #10;

    a <= 10;
    b <= 7;
    op <= 2'b01; // OR_XOR_AND: (10 | 7) ^ (10 & 7) = 15 ^ 2
= 13 (flag = 1)
    #20;

    reset <= 1;
    #30;

    $finish();
end
endmodule

```

alu_testbench.v

```

`timescale 1ns/1ns

module alu_tb;
    reg [5:0] A, B;
    reg [1:0] OP;
    wire [5:0] R;
    wire alu_flag ;

    ALU uut (
        .A(A),

```



```

        .B(B),
        .OP(OP),
        .R(R),
        .alu_flag(alu_flag)
    );

    initial begin
        $dumpfile("alu_tb.vcd");
        $dumpvars(0, alu_tb);

        A = 6'b000100; B = 6'b000011; OP = 2'b00;
        #10;

        A = 6'b000100; B = 6'b000010; OP = 2'b01;
        #10;

        A = 6'b000111; B = 6'b000010; OP = 2'b10;
        #10;

        A = 6'b000110; B = 6'b000001; OP = 2'b11;
        #10;

        A = 6'b000111; B = 6'b000111; OP = 2'b00;
        #10;

        A = 6'b000001; B = 6'b000111; OP = 2'b01;
        #10;

        $finish;
    end

    initial begin
        $monitor("Time=%0t A=%b B=%b OP=%b -> R=%b
alu_flag=%b", $time, A, B, OP, R, alu_flag);
    end

endmodule

```

controller_testbench.v

```

`timescale 1ns/1ns

module controller_tb;
    reg clk;
    reg reset;
    reg start;

```

```

reg [5:0] a;
reg [5:0] b;
reg [1:0] op;
reg [5:0] alu_out;
reg alu_flag;
wire [5:0] alu_in1;
wire [5:0] alu_in2;
wire [1:0] alu_op;
wire [5:0] result;
wire flag;

controller dut (
    .clk(clk),
    .reset(reset),
    .start(start),
    .a(a),
    .b(b),
    .op(op),
    .alu_out(alu_out),
    .alu_flag(alu_flag),
    .alu_in1(alu_in1),
    .alu_in2(alu_in2),
    .alu_op(alu_op),
    .result(result),
    .flag(flag)
);

initial begin
    clk = 0;
    forever #5 clk = ~clk;
end

// Stimulus
initial begin

    reset = 0;
    start = 0;
    a = 6'd0;
    b = 6'd0;
    op = 2'b00;
    alu_out = 6'd0;
    alu_flag = 0;

    #10;
    reset = 1;

```

```

        #10;
        reset = 0;
        start = 1;
        a = 6'd5;
        b = 6'd3;
        op = 2'b00;
        alu_out = 6'd8; // Addition: 5 + 3
        alu_flag = 1;

        #15;
        a = 6'd0;
        b = 6'd0;
        op = 2'b00;
        alu_out = 6'd0; // Addition: 0 + 0
        alu_flag = 0;

        #10;
        a = 6'd10;
        b = 6'd7;
        op = 2'b01;
        alu_out = 6'd13; // OR_XOR_AND: (10 | 7) ^ (10 & 7) =
15 ^ 2 = 13
        alu_flag = 1;

        #20;
        $finish;
    end

    initial begin
        $monitor("Time=%0t | clk=%b | reset=%b | start=%b |
a=%d | b=%d | op=%b | alu_out=%d | alu_flag=%b | alu_in1=%d |
alu_in2=%d | alu_op=%b | result=%d | flag=%b",
                $time, clk, reset, start, a, b, op, alu_out,
alu_flag, alu_in1, alu_in2, alu_op, result, flag);
    end

    initial begin
        $dumpfile("controller_tb.vcd");
        $dumpvars(0, controller_tb);
    end

```

```
endmodule
```


RTL Timing Diagram:

Check List: Have you added all the timing diagrams of ALU_TESTBENCH, CONTROLLER_TESTBENCH, TOP_TESTBENCH?


YES

NB: Failing to add any required info will cause point penalty (1-2 Marks)


alu_tb.v

 

controller_tb.v

 

top_tb.v

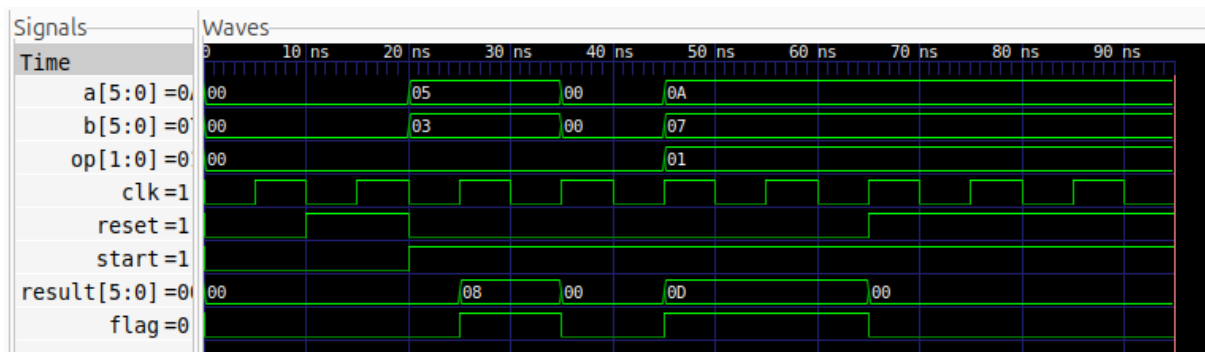

RTL Synthesis (130nm Skywater PDK with OpenLane toolchain):

Check List: Have you added RTL synthesis summary, RTL synthesized design figure and Standard cell usage in synthesized design?

YES

NB: Failing to add any required info will cause point penalty (1-2 Marks)

RTL synthesis summary **(Following table is showing what info need to be shown /Just copy paste these info from terminal here)**

post_dff.rpt:

Metric	Count
Number of Wires	103
Number of wire bits	123
Number of public wires	10
Number of public wire bits	30
Number of ports	8
Number of port bits	24
Number of memories	0
Number of memory bits	0
Number of processes	0
Number of cells	106


stat.rpt:

Metric	Count
Number of Wires	58
Number of wire bits	74
Number of public wires	11
Number of public wire bits	27
Number of ports	8
Number of port bits	24
Number of memories	0
Number of memory bits	0
Number of processes	0
Number of cells	57


RTL synthesized design figure (Following figure is showing what info need to be shown /Just copy paste these figures)

There will be 2 figures in 2 .dot files in the synthesis folder. Show them both.

xdot primitive_techmap.dot :

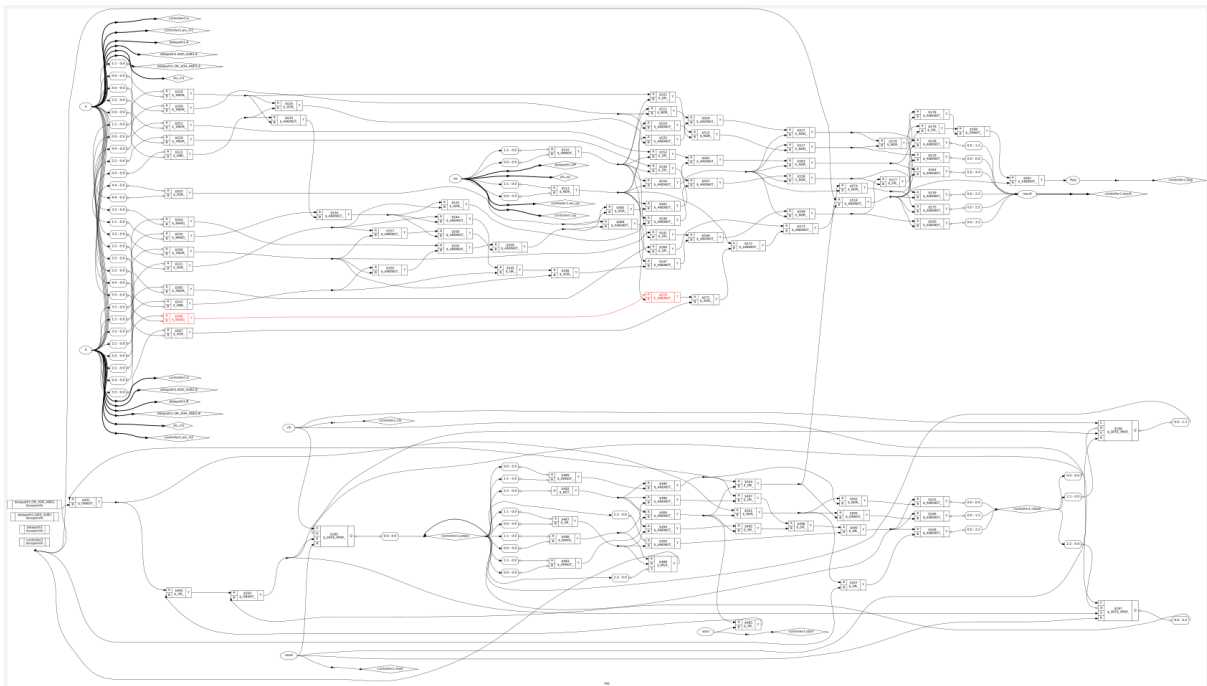

xdot hierarchy.dot :

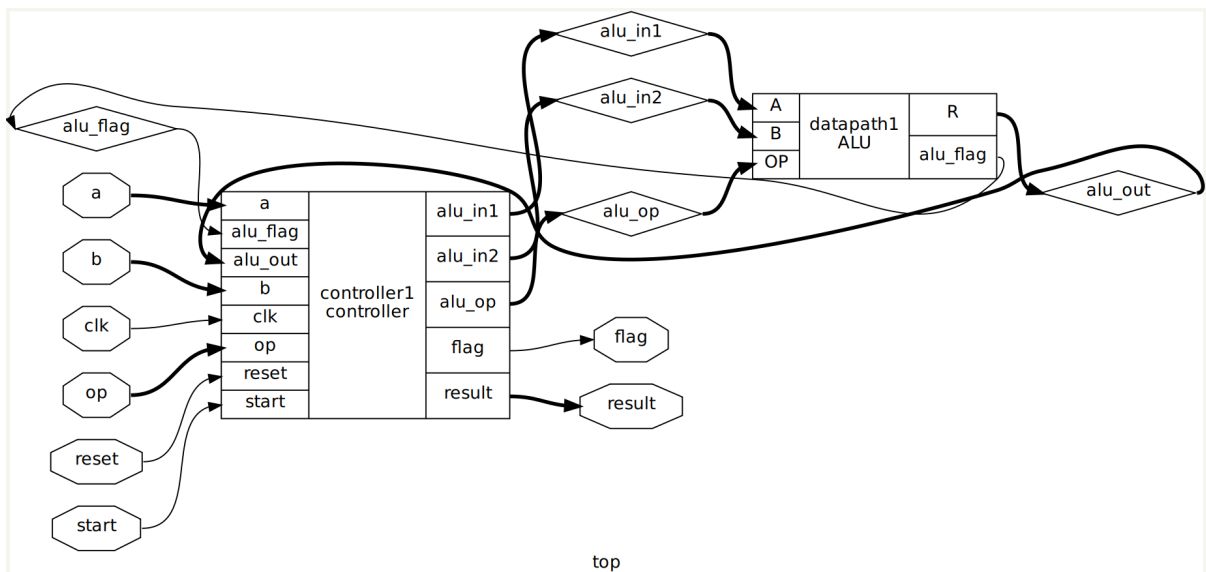

Standard cell usage in synthesized design (Following table is showing what info need to be shown /Just copy paste these info from terminal here)

Cell name	Count
sky130_fd_sc_hd_a211o_2	1
sky130_fd_sc_hd_a21o_2	1
sky130_fd_sc_hd_a21oi_2	2
sky130_fd_sc_hd_a22o_2	2
sky130_fd_sc_hd_a311o_2	1
sky130_fd_sc_hd_a31o_2	2
sky130_fd_sc_hd_a32o_2	1
sky130_fd_sc_hd_a41o_2	1
sky130_fd_sc_hd_and2_2	3
sky130_fd_sc_hd_and3_2	4
sky130_fd_sc_hd_and3b_2	2
sky130_fd_sc_hd_and4_2	1
sky130_fd_sc_hd_dfrtp_2	3
sky130_fd_sc_hd_inv_2	8
sky130_fd_sc_hd_mux2_1	1
sky130_fd_sc_hd_nand2_2	4
sky130_fd_sc_hd_nand4_2	1
sky130_fd_sc_hd_nor2_2	2
sky130_fd_sc_hd_o211a_2	1
sky130_fd_sc_hd_o21a_2	1
sky130_fd_sc_hd_o21ai_2	1
sky130_fd_sc_hd_o31ai_2	1
sky130_fd_sc_hd_or2_2	5
sky130_fd_sc_hd_or4_2	1
sky130_fd_sc_hd_or4bb_2	1
sky130_fd_sc_hd_xnor2_2	4
sky130_fd_sc_hd_xor2_2	2

RTL Floorplan (130nm Skywater PDK with OpenLane toolchain)

Check List: Have you added RTL Floorplan info?	YES
NB: Failing to add any required info will cause point penalty (1-2 Marks)	

(Following table is showing what info need to be shown /Just copy paste these info from terminal here)

General RTL Floorplan Information		
Parameter	Value	Unit
Database Units(DBU)	?	--
Site Size	(2.72, 0.46)	µm
Die Area (BBox)	(0.0 0.0) to (48.14 58.86)	µm
Core Area(BBox)	(5.52 10.88) to (42.32 46.24)	µm

Core Area	1301.25	µm2
Placement Utilization	?	%

Openroad_floorplan.log:

```
1 Reading library file at '/foss/pdks/sky130A/libs.ref/sky130_fd_sc_hd/lib/sky130_fd_sc_hd_tt_025C_1v00.lib'...
2 Reading technology LEF file at '/foss/pdks/sky130A/libs.ref/sky130_fd_sc_hd/techlef/sky130_fd_sc_hd_nom.tlef'...
3 [INFO ODB-0227] LEF file: /foss/pdks/sky130A/libs.ref/sky130_fd_sc_hd/techlef/sky130_fd_sc_hd_nom.tlef, created 14 layers, 25 vias
4 Reading cell LEF file at '/foss/pdks/sky130A/libs.ref/sky130_fd_sc_hd/lef/sky130_fd_sc_hd.lef'...
5 [WARNING ODB-0220] WARNING (LEFPARS-2008): NOWIREEXTENSIONATPIN statement is obsolete in version 5.6 or later.
6 The NOWIREEXTENSIONATPIN statement will be ignored. See file /foss/pdks/sky130A/libs.ref/sky130_fd_sc_hd/lef/sky130_fd_sc_hd.lef at line 2.
7
8 [INFO ODB-0227] LEF file: /foss/pdks/sky130A/libs.ref/sky130_fd_sc_hd/lef/sky130_fd_sc_hd.lef, created 437 library cells
9 Reading cell LEF file at '/foss/pdks/sky130A/libs.ref/sky130_fd_sc_hd/lef/sky130_ef_sc_hd.lef'...
10 [WARNING ODB-0220] WARNING (LEFPARS-2008): NOWIREEXTENSIONATPIN statement is obsolete in version 5.6 or later.
11 The NOWIREEXTENSIONATPIN statement will be ignored. See file /foss/pdks/sky130A/libs.ref/sky130_fd_sc_hd/lef/sky130_ef_sc_hd.lef at line 2.
12
13 [INFO ODB-0227] LEF file: /foss/pdks/sky130A/libs.ref/sky130_fd_sc_hd/lef/sky130_ef_sc_hd.lef, created 4 library cells
14 Reading top-level netlist at '/foss/designs/assignment/runs/RUN_2025-06-13_04-36-13/06-yosys-synthesis/top.nl.v'...
15 Linking design 'top' from netlist...
16 Reading design constraints file at '/usr/local/lib/python3.12/dist-packages/openlane/scripts/base.sdc'...
17 [WARNING] No CLOCK PORT found. A dummy clock will be used.
18 [WARNING STA-0366] port ' _VIRTUAL_CLK_ ' not found.
19 [INFO] Using clock ' _VIRTUAL_CLK_ '
20 [INFO] Setting output delay to: 2.0
21 [INFO] Setting input delay to: 2.0
22 [WARNING STA-0366] port ' _VIRTUAL_CLK_ ' not found.
23 [INFO] Setting load to: 0.033442
24 [INFO] Setting clock uncertainty to: 0.25
25 [INFO] Setting clock transition to: 0.149999999999999994488848768742172978818416595458984375
26 [WARNING STA-0419] transition time can not be specified for virtual clocks.
27 [INFO] Setting timing derate to: 5%
28 [WARNING STA-0450] virtual clock ' _VIRTUAL_CLK_ ' can not be propagated.
29 Using site height: 2.72 and site width: 0.46...
30 [INFO] Using relative sizing for the floorplan.
31 [INFO IFP-0001] Added 13 rows of 80 site unithd.
32 [INFO IFP-0030] Inserted 0 tiecells using sky130_fd_sc_hd_conb_1/L0.
33 [INFO IFP-0030] Inserted 0 tiecells using sky130_fd_sc_hd_conb_1/HI.
34 [INFO] Extracting DIE AREA and CORE AREA from the floorplan
35 [INFO] Floorplanned on a die area of 0.0 0.0 48.14 58.86 (µm).
36 [INFO] Floorplanned on a core area of 5.52 10.88 42.32 46.24 (µm).
37 Writing metric design _die_bbox: 0.0 0.0 48.14 58.86
38 Writing metric design _core_bbox: 5.52 10.88 42.32 46.24
39 Setting global connections for newly added cells...
40 [INFO] Setting global connections...
41 Updating metrics...
42 Cell type report:
43 Inverter                      Count      Area
44 Sequential cell               3          78.83
45 Multi-Input combinational cell 46         441.67
46 Total                         57         550.53
47 Writing OpenROAD database to '/foss/designs/assignment/runs/RUN_2025-06-13_04-36-13/13-openroad-floorplan/top.odb'...
48 Writing netlist to '/foss/designs/assignment/runs/RUN_2025-06-13_04-36-13/13-openroad-floorplan/top.nl.v'...
49 Writing powered netlist to '/foss/designs/assignment/runs/RUN_2025-06-13_04-36-13/13-openroad-floorplan/top.pnl.v'...
50 Writing layout to '/foss/designs/assignment/runs/RUN_2025-06-13_04-36-13/13-openroad-floorplan/top.def'...
51 Writing timing constraints to '/foss/designs/assignment/runs/RUN_2025-06-13_04-36-13/13-openroad-floorplan/top.sdc'...
```

Or_metrics_out.json:

Open or_metrics_out.json Save

```
1 {
2   "design_die_bbox": "0.0 0.0 48.14 58.86",
3   "design_core_bbox": "5.52 10.88 42.32 46.24",
4   "design_io": 24,
5   "design_die_area": 2833.52,
6   "design_core_area": 1301.25,
7   "design_instance_count": 57,
8   "design_instance_area": 550.528,
9   "design_instance_count_stdcell": 57,
10  "design_instance_area_stdcell": 550.528,
11  "design_instance_count_macros": 0,
12  "design_instance_area_macros": 0,
13  "design_instance_utilization": 0.423077,
14  "design_instance_utilization_stdcell": 0.423077,
15  "design_instance_count_class:inverter": 8,
16  "design_instance_count_class:sequential_cell": 3,
17  "design_instance_count_class:multi_input_combinational_cell": 46,
18  "flow_warnings_count": 6,
19  "flow_errors_count": 0
20 }
```

RTL Power Analysis (130nm Skywater PDK with OpenLane toolchain)

Check List: Have you added RTL Power Analysis info?	YES
NB: Failing to add any required info will cause point penalty (1-2 Marks)	

(Following table is showing what info need to be shown /Just copy paste these info from terminal here)

Group	Internal Power	Switching Power	Leakage Power	Total Power (Watts)	
Sequential	4.842016e-06	5.543969e-06	3.768916e-11	1.038602e-05	13.2%
Combinational	2.520306e-05	4.297765e-05	2.475429e-10	6.818095e-05	86.8%
Clock	0.000000e+00	0.000000e+00	2.041229e-10	2.041229e-10	0.0%
Macro	0.000000e+00	0.000000e+00	0.000000e+00	0.000000e+00	0.0%
Pad	0.000000e+00	0.000000e+00	0.000000e+00	0.000000e+00	0.0%
Total	3.004508e-05	4.852161e-05	4.893550e-10	7.856718e-05	100.0%
	38.2%	61.8%	0.0%		

GDS Layout (130nm Skywater PDK with OpenLane toolchain)

Check List: Have you added the heatmap?	YES
NB: Failing to add any required info will cause point penalty (1-2 Marks)	

(Following figure is showing what info need to be shown /Just copy paste these figures)

